

Project Submitted in Partial Fulfillment of the Requirements for Ensc 350 Towards a Bachelor Degree in Engineering Science.

Last Name:  ALIZRAEE	Last Name:  Umuraliyer	Last Name:  MARTLN			
SID: 3 0 1 4 5	SID: 30138	SID: 30144			
5 2 5 1	5064	5106			

# **Table Of Contents**

Table Of Contents	2
Part 1: The R&D "Business Style" Report	4
Introduction to Business Section	4
Group Organization	4
Time Management	5
Conclusion	6
Part 2: The Design "Technical Style" Report	6
Introduction to Technical Design	6
Methodology	6
Technical Section: Documenting Prototype Design	7
FPGA Implementation (Prediction)	7
Ripple Carry Adder (64-bit)	7
Carry Skip Adder (64-bit)	8
Brent-Kung Adder (64-bit)	8
Time Performance and Cost-Effectiveness Analysis (Prediction)	8
Ripple Carry Adder ( 64 bit )	8
Performance (Propagation Delay) Predicted	9
2. Cost (Hardware Gates)	9
Cost-Performance Ratio	10
Carry Skip Adder (64 bit)	11
Unique Features:	11
Performance (Propagation Delay) Predicted	11
2. Cost (Hardware Gates)	13
Cost-Performance Ratio	13
Brent-Kung Adder (64-bit)	13
Performance (Propagation Delay) Predicted	13
2. Cost (Hardware Gates)	14
Cost-Performance Ratio	14
Technical Section: Documenting Testing Procedures	15
Adder Testing:	15
Expectations and Observations	17
Brent-Kung adder:	19
Carry Skip Adder:	22
Testing Procedures:	26
Technical Section: Documenting Analysis of Results	27
Measured/Observed Results:	27
Ripple-Carry Adder	28
Timing Metrics:	28

	Observations:	28
	Carry-Skip Adder (CSA)	29
	Timing Metrics:	29
	Observations:	29
	Brent-Kung Adder	30
	Discussion:	30
	General Analysis	31
	Performance and Cost Comparison Table	31
	Explanation of Results	32
	Why Ripple-Carry Adder Turned Out to Be the Most Efficient	32
	Assessment of Calibration Strategy for Implementation Cost	32
	Assessment of Metrics and Measurement Methods	33
	Conversion Ratio Calculation and Sensibility Analysis	34
	Step 1: Establish Conversion Ratio	34
	Step 2: Normalize ALM Usage for Each Design	34
	Step 3: Recalculate Cost-Performance Ratios	34
	Step 4: Reasonableness Compared to Baseline	35
	Adequacy of Measurement Methods and Units	35
	Detailed Explanation of Metrics	35
	Test Vector Selection Strategy (SVM5:)	36
Sour	ce Code Files	38

# Part 1: The R&D "Business Style" Report

## **Introduction to Business Section**

In this section, we reflect on the business aspects of our project, focusing on team organization, time management, and resource allocation. The project involved designing three adder circuits—Ripple Carry Adder, Carry Skip Adder, and Brent-Kung Adder—each with different trade-offs in performance and complexity. Our team faced challenges in managing the project timeline, leading to last-minute work, but we gained valuable insights into the importance of realistic planning and early task delegation. Tools like Quartus for FPGA synthesis, ModelSim for simulation, and GitHub for version control played a key role in optimizing our workflow and communication. This section highlights the lessons we learned regarding collaboration, efficient resource use, and the need for proactive planning to ensure smoother project execution in the future.

## **Group Organization**

For this project our team designed three circuits. James Martin (jrm22) and Daniyar designed Brent-Kung with the help of Lucky, Daniel Alizraee (daa36) also later modified it to Carry Skip Adder. Daniyar Umuraliyev (dumurali) designed the initial Ripple Adder. Apart from this, all 3 members of the team worked on the previous design iterations.

In terms of simulation, James Martin took the lead in designing and improving the testbench. Daniyar Umuraliyev was responsible for preparing the timing simulation, while Daniel Alizraee extracted values and performed calculations for the report. Daniel also played a primary role in writing the business portion of the report.

The lab work progressed relatively smoothly, with good communication among team members. Although there were a few moments of miscommunication due to differing understandings of the requirements, the overall division of labor was fair and balanced.

## Time Management

Our project timeline was poorly managed, which significantly affected our progress. Unfortunately, we delayed most of our work until the final weekend, resulting in 8-12 hour days in the lab as the submission deadline approached. Initially, we had estimated that the project would take no more than 12 hours of constant work, but the reality was quite different. In total, we ended up spending three times as long on the project. With better time management and a

more thorough review of the lab material earlier on, we likely could have completed the assignment in less time.

Additionally, we began work on the remake of the lab even before the DP1 results were made available. We had anticipated that this would take longer than previously expected, which turned out to be a reasonable estimate based on the actual time spent. A significant portion of the time was spent redesigning the Carry Look Ahead (CLA) adder into a Brent-Kung Adder as well as making optimizations to the report and the test bench, as our understanding of the simulation requirements improved over time.

## **Resource Management**

In terms of computational resources, the main tools used were simulation softwares such as Quartus and Modelsim and hardware description languages like VHDL. The testbench design, in particular, relied heavily on simulation tools to verify the performance of each adder circuit. By optimizing the testbench for faster execution, we could have reduced the time spent troubleshooting and validating our circuits. We also used discord and github to manage our personal directories, ensuring that the team could work on separate tasks without risk of overwriting each other's progress. This approach helped in resource management by maintaining version history. We also met in the ASB lab room for most of the work done on this project so we were able to keep track of what each other were working on via in-person verbal and visual communication.

One of the major limitations we faced was poor time management and planning. Due to the delayed start, we ended up working long hours in the lab right before the submission deadline. This resulted in inefficiency, as the project turned out to be more time-consuming than initially anticipated. A more realistic timeline was put in place for the DP1 Lab revision, in which we began almost right away and chipped away at the project every Tuesday and Thursday lab session, accumulating help as needed from the TA's and the Professor.

#### Conclusion

Despite facing challenges related to time management, our group gained valuable insights throughout the project. We learned the importance of thorough planning, early task allocation, and more efficient resource management to streamline the process and achieve better results in less time. By using tools like Quartus, ModelSim, Discord, and GitHub, we were able to optimize our workflow and collaborate effectively. However, a more proactive approach to the lab material, along with better coordination and clearer communication, would have allowed us to minimize last-minute efforts and reduce time spent troubleshooting.

# Part 2: The Design "Technical Style" Report

## **Introduction to Technical Design**

This report examines the implementation and performance analysis of three distinct 64-bit adder architectures: the Ripple Carry Adder (RCA), the Carry Skip Adder (CSA), and the Brent-Kung Adder (BKA). Using simulation tools such as ModelSim and Quartus, we evaluated each adder based on key metrics, including timing performance, propagation delay, area utilization, and overall cost-effectiveness. The goal of this study is to highlight the trade-offs between speed, cost, and complexity, thereby offering insights into the most suitable adder architecture for high-performance applications.

During the technical design phase, the focus was on implementing these three adder architectures and analyzing their performance under practical constraints. Emphasis was placed on optimizing for both speed and cost-effectiveness, with particular attention to propagation delay and area utilization. Ensuring that the designs met the timing requirements of a 64-bit structure was also a crucial aspect, as it directly impacts scalability and overall system performance. The results of this study aim to provide a clear comparison of the three adder architectures, helping to determine the best choice for various application scenarios based on their respective performance characteristics.

Our primary goal is to deliver a comprehensive understanding of the theoretical and practical considerations behind each adder design. This includes evaluating the trade-offs between performance, cost, and speed efficiency, and explaining the rationale behind selecting the Ripple Carry Adder, Carry Skip Adder, and Brent-Kung Adder for this analysis. Through this report, we aim to offer valuable insights into how these design choices influence both theoretical frameworks and real-world applications.

## Methodology

The exploration of adder types in this project required background knowledge of different designs with an emphasis on their performance characteristics and suitability for various applications. This involved a review of essential design principles and research on carry propagation techniques, such as how each design manages speed vs cost.

To understand the benefits and limitations of each adder type, the Ripple Carry Adder (RCA), Carry Skip Adder (CSA), and Brent Kung Adder (BKA) were researched in terms of their technique and circuitry. The RCA is the most simple design of the three and is purely sequential, which means simplicity but at the cost of linear propagation delay. The CSA was chosen for its potential to reduce delay through selective carry bypassing, which is slower than BKA but less expensive as well. Finally the BPK, which can compute carry values in parallel, minimizing delay growth as operand sizes increase but gets increasingly expensive.

Through this methodology, the project established a foundation for evaluating each adder's effectiveness in balancing speed, area, and complexity, providing a theoretical basis for more detailed design and testing. This approach gave a perspective on the cost-effectiveness of adders and their role in high-speed computational tasks, forming the groundwork for the practical evaluation in Part 2.

ModelSim has the features to create and run testbenches, allowing detailed simulation of data interactions within each adder design. This simulation environment supports thorough validation of logical operations, as it enables observing and verifying how each adder handles different inputs and calculates outputs. ModelSim provides access to features that analyze waveforms, ensuring that each adder correctly propagated carry bits and generated accurate sums under varying conditions, which was important for functional verification. Quartus complemented this with advanced features like the RTL Viewer, which enabled a clear visual representation of the synthesized design's structure. By using the RTL Viewer, we could assess each adder's gate-level implementation and gain insights into its cost and complexity.

## **Technical Section: Documenting Prototype Design**

### **FPGA Implementation (Prediction)**

In FPGA design, various optimizations can help reduce the number of LUTs required. FPGA synthesis tools often combine logic operations where possible, optimizing the overall design and minimizing the number of LUTs used. The specific architecture of the FPGA also impacts LUT usage. FPGAs with larger LUTs, such as 6-input LUTs, allow for more efficient logic combination than FPGAs with smaller LUTs. The architecture also influences how well certain types of logic are mapped to the available LUTs. The FPGA routing network plays a significant role in overall design performance, as more complex designs might need more routing resources. While the number of LUTs may be optimized, complex designs, such as those with parallel carry propagation or additional multiplexers, often require additional routing resources. For the LUT estimates below, we will assume a baseline case without optimizations, on the Cyclone IV architecture.

#### Ripple Carry Adder (64-bit)

For the Ripple Carry Adder, no flip-flops should be used in the implementation, because the circuit is entirely combinational, which does not make use of registers/clocks. This leads to no register usage and keeps the area utilization low, but the sequential carry propagation limits performance. For a simple 1-bit adder, the logic consists of two primary operations: XOR for the sum and a combination of AND/OR gates for the carry. Thus, a single bit of the RCA can be implemented with **2 LUTs** (one for the XOR operation and another for the AND/OR logic). For a 64-bit RCA, the total number of LUTs required would be **128 LUTs** (64 for sum generation and 64 for carry propagation).

#### Carry Skip Adder (64-bit)

Again, for the Carry Skip Adder, no flip-flops should be used in the implementation, because the circuit is entirely combinational. This leads to no register usage and keeps the area utilization low, but the sequential carry propagation still limits performance. Similar to the RCA, each bit in the CSA requires an XOR gate for the sum. However, to implement the carry skip functionality, additional logic is needed. Each bit may require **3-4 LUTs**: one for the XOR sum,

and two for the carry generation and multiplexing logic that decides when to skip the carry. Therefore, for a 64-bit CSA, the total number of LUTs would be approximately **192 to 256 LUTs** (64 bits, each using 3 to 4 LUTs).

#### **Brent-Kung Adder (64-bit)**

Again, for the Brent-Kung Adder, no flip-flops should be used in the implementation, because the circuit is entirely combinational. This leads to no register usage. The BKA is more complex than both the RCA and CSA due to its parallel structure for carry propagation. Each stage in the carry tree involves additional logic to propagate carry bits through parallel paths. As a result, the number of LUTs per bit increases compared to the RCA and CSA. For a 64-bit BKA, a rough estimate might be around **192 to 320 LUTs**, The parallel nature of the BKA adds to the number of LUTs required, making it the most complex adder in terms of LUT usage

We will compare our predicted results with the observed results during the Documenting Analysis of Results section.

### **Time Performance and Cost-Effectiveness Analysis (Prediction)**

### Ripple Carry Adder (64 bit)

The Ripple Carry Adder (RCA) is the simplest type of adder used for binary addition. It operates by calculating the sum of each bit sequentially, where each bit's sum depends on the carry generated by the previous bit. This design is relatively straightforward but is known for its slow performance, especially when handling large operands, due to the carry propagation delay.

The RCA adds two numbers bit by bit, starting from the least significant bit (LSB) and propagating the carry through each subsequent bit. For each bit, a full adder is used to generate the sum and carry. The key characteristic of the RCA is the ripple effect, where each carry must propagate through all previous stages, resulting in a delay that increases linearly with the number of bits. The adder's performance is dominated by the propagation of carries, which results in an O(n) time complexity for a n-bit adder. For example, in a 64-bit adder, each carry bit must travel across all 64 bits before the final sum is produced.

The main benefit for Ripple is that it should have a better performance than the Ripple Adder and it should have a significantly lower cost than the Brent-Kung Adder. It serves as a balance between cost and performance.

#### **Unique Features:**

- Simple Design: The RCA is the simplest adder with minimal complexity.
- Sequential Carry Propagation: Each bit depends on the carry from the previous one, which leads to increased delay as the operand size grows.

- Low Hardware Cost: Each bit requires only basic logic gates to compute sum and carry, making it inexpensive in terms of hardware resources.

#### 1. **Performance** (Propagation Delay) **Predicted**

**Speed:** The ripple carry adder is expected to have a high propagation delay, particularly when working with larger bit-widths, as each carry bit must travel through all preceding stages before producing the final sum.

**Area Utilization:** The area is relatively small, as the design is simple and does not require additional logic to bypass carries. However, the sequential nature of the RCA means that the circuit must process each carry bit one at a time.

**Complexity:** The design complexity is minimal due to the lack of advanced carry propagation techniques.

The Ripple Carry Adder computes the carry sequentially from the least significant bit (LSB) to the most significant bit (MSB). This means:

Propagation Delay = N, the total number of bits in the adder.

For a 64-bit Ripple Carry Adder:

Total Delay = 64 logic levels (since carry propagation is linear across all 64 bits).

Result: The propagation delay is **64 logic levels**.

2. **Cost** (Hardware Gates)

The hardware cost for a Ripple-Carry Adder is straightforward:

- Each bit requires one full adder, which consists of logic gates for sum and carry computation.
- A single full adder typically requires:
  - 2 XOR gates for the sum.
  - 2 AND gates and 1 OR gate for the carry.

Thus, for each bit:

Gate Count per Bit = 2 (XOR) + 2 (AND) + 1 (OR) = 5 gates.

For 64 bits:

Total Cost =  $64 \times 5 = 320$  gates.

Result: The hardware cost is approximately **320 gates**.

#### 3. Cost-Performance Ratio

The cost-performance ratio is calculated as the total cost divided by the propagation delay:

Cost-Performance Ratio = Total Cost ÷ Propagation Delay:

=  $320 \div 64 = 5$  cost units per logic level.

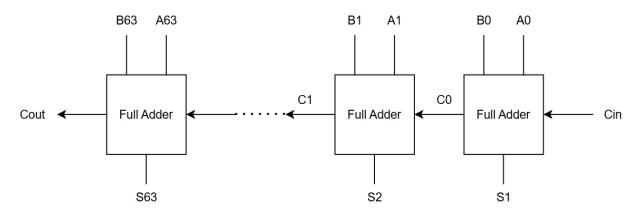


Figure 1: Ripple Carry Adder

#### Contamination Delay (CD):

- Contamination delay is minimal as it is dominated by the first gate in the chain.
- Predicted CD = t\_gate

#### Propagation Delay (PD):

- Propagation delay accumulates as the carry signal ripples through all 64 stages.
   Each stage introduces a delay of t\_gate.
- o Predicted PD = 64 \* t\_gate

Let t\_gate = 3.5 ns for theoretical calculations:

Predicted CD = 3.5 ns Predicted PD = 64 \* 3.5= 224 ns

## Carry Skip Adder (64 bit)

The **Carry Skip Adder (CSA)** improves upon the Ripple Carry Adder by introducing a method for "skipping" over certain carry bits when conditions allow. The CSA reduces the total propagation delay by grouping bits and bypassing certain stages where the carry does not need to propagate.

The CSA is divided into smaller groups of bits. When a carry bit is generated, if it is skip-able (i.e., it does not affect the sum of certain bits), the carry will skip over groups of bits, effectively reducing the carry propagation time. This design allows for faster computation compared to the RCA, as the carry only propagates through parts of the adder where necessary. The delay for each group is logarithmic, meaning that larger groups reduce the delay compared to the RCA. However, the CSA still requires logic to detect when to skip, which adds to its complexity.

The main benefit for Carry Skip Adder is that it should have a better performance than the Ripple Adder and it should have a significantly lower cost than the Brent-Kung Adder. It serves as a balance between cost and performance.

#### **Unique Features:**

- **Optimized for Speed**: The carry is propagated in groups, and certain carry bits can be skipped, reducing the delay.
- **Increased Hardware Complexity**: More logic gates are required to manage the carry-skipping mechanism, including multiplexers and carry propagate networks.
- **Faster than RCA**: While still not as fast as more advanced adders like the BKA, the CSA offers a significant improvement over the RCA.

#### 1. Performance (Propagation Delay) Predicted

**Speed:** The CSA is faster than the RCA, as it can skip over certain carry stages when conditions allow. However, the improvement in speed comes at the cost of some added complexity in the design.

**Area Utilization:** The area utilization increases compared to the RCA, as more logic is needed to determine when to skip carry bits and when to propagate them fully.

**Complexity:** The complexity is higher than the RCA due to the additional logic for carrying and skipping, but it still remains simpler than more advanced adders.

The Carry Skip Adder reduces carry propagation delay by dividing the adder into groups of bits and "skipping" over groups when possible. For a 64-bit adder divided into 4 groups of 16 bits each:

- 1. Delay for carry propagation within each group is proportional to the logarithm of the group size:
  - Logarithmic delay for a 16-bit group =  $log_2(16) = 4 logic levels$ .
- 2. Delay for skipping between the 4 groups is linear with the number of groups:
  - Delay for skipping 4 groups = 4 logic levels.

Total Delay = delay within a group + delay for skipping groups:

• Total Delay = 4 (intra-group) + 4 (inter-group) = 8 logic levels.

Result: The propagation delay is approximately 8 logic levels.

The critical path of a Carry-Skip adder propagates through the first and the last blocks, and skips the intermediate blocks. If we design an adder with N bits and B blocks, then each block must contain N/B bits. The critical path can be calculated as:

$$t_{pd} = Kt_{carry} + (\frac{N}{K} - 1)t_{mux} + (K - 1)t_{carry} + t_{sum}$$

Where: $t_{\it carry}$  is the propagation delay of the first block's carry chain.

$$(\frac{N}{K}-1)t_{mux}^{}$$
 : the delay of multiplexers,

 $(K-1)t_{carry}$  and  $t_{sum}$ : the time required to calculate the sum in the last block.

For the case where we have 64-bits, the optimal number of Carry-Skip block can be simplified to:  $Optimal \#Blocks = \sqrt{64} = 8 \ blocks$ .

Using the Cyclone IV provided datasheet, we can calculate the average expected delays.

		Number of Settings	Min Offset	Max Offset						
Parameter	Paths Affected			Fast Corner		Slow Corner				Unit
				C6	17	C6	<b>C</b> 7	C8	17	
Input delay from pin to internal cells	Pad to I/O dataout to core	7	0	1.314	1.210	2.209	2.398	2.526	2.443	ns
Input delay from pin to input register	Pad to I/O input register	8	0	1.313	1.208	2.205	2.406	2.563	2.450	ns
Delay from output register to output pin	I/O output register to pad	2	0	0.461	0.421	0.789	0.869	0.933	0.884	ns
Input delay from dual-purpose clock pin to fan-out destinations	Pad to global clock network	12	0	0.712	0.682	1.225	1.407	1.562	1.421	ns

According to the provided table, the maximum input-to-output delay is  $2.563 + 0.933 = 3.496 \, ns$ 

Then the propagation delay of the skip-adder can be calculated as:

$$t_{nd} = 8(8 \times 3.496 \, ns) + (\frac{64}{8} - 1)(3.496) + (8 - 1)(8 \times 3.496 \, ns) + 3.496 \, ns = 447.488 \, ns$$

#### 2. Cost (Hardware Gates)

The Carry Skip adder contains the following main entities:

- Full adders: each contains 3 logic gates.
- Multiplexers.
- Generate Propagate network: contains 128 logic gates.

Total number of Full adders = 64.

Total number of Mux = 8.

 $Total \ cost = (64 \times 3) + 8 + 64 = 264 \ gates$ 

#### 3. Cost-Performance Ratio

The cost-performance ratio is calculated as the total cost divided by the propagation delay:

Cost-Performance Ratio = Total Cost ÷ logic Delay:

Where logic delay = 
$$\frac{447.488}{3.496}$$
 = 128

• Cost-Performance Ratio =  $\frac{264}{128}$  = 2.1 *Logic Levels*.

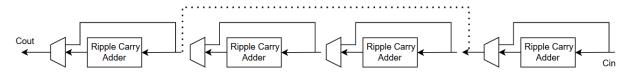


Figure 2: Carry Skip Adder

### **Brent-Kung Adder (64-bit)**

The Brent-Kung Adder (BKA) is designed to reduce carry propagation delay by implementing a parallel computation method. It utilizes a tree-like structure to propagate carry bits through parallel paths, drastically reducing the delay as compared to the RCA and CSA. However, this parallel structure increases the area and complexity of the design, making it more expensive in terms of both hardware and implementation effort.

#### 1. Performance (Propagation Delay) Predicted

**Speed:** The BKA is expected to be the fastest adder among the three due to its parallel carry propagation. The delay grows logarithmically with the operand size, rather than linearly as in the RCA.

**Area Utilization:** The area for the BKA is significantly larger than that of the RCA and CSA, as it requires additional logic for managing parallel carry paths.

**Complexity:** The BKA is more complex than both the RCA and CSA due to its advanced parallel carry computation, making it more challenging to implement.

The propagation delay of a Brent-Kung adder grows logarithmically with the number of bits:

• 
$$Delay \approx 2log_2(K) - 2$$

For a 64-bit adder:

•  $Delay \approx 2log_2(64) - 2 = 10 logic levels.$ 

Each logic level represents a layer of computation involving basic gates (AND, OR).

Result: The propagation delay is 10 logic levels.

#### 2. Cost (Hardware Gates)

The hardware cost of the Brent-Kung adder scales as:

• 
$$Cost \approx 2K - 2 - log_2 K$$

For a 64-bit adder:

• 
$$Cost \approx 2(64) - 2 - log_2(64) = 120 Gates$$

This accounts for gates used to compute propagate/generate signals and their hierarchical combination.

• Result: The hardware cost is approximately 384 gates.

#### 3. Cost-Performance Ratio

The cost-performance ratio evaluates the cost per unit of delay:

Cost-Performance Ratio = Cost ÷ Delay

For the 64-bit Brent-Kung adder:

• Cost-Performance Ratio = 120 ÷ 10 = 12 cost units per logic level.

This indicates the hardware efficiency per unit of delay.

Total Delay = Total Levels \* t\_gate = 3.5 ns.


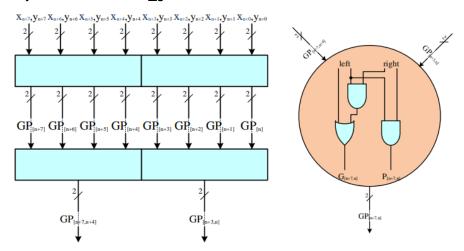


Figure 3: Brent-Kung network (Taken from Lakshman One's notes)

## **Technical Section: Documenting Testing Procedures**
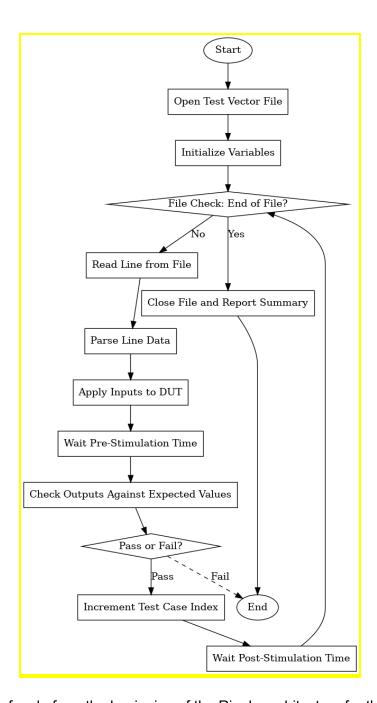
## Adder Testing:

This testing procedure below describes both functional and timing testing. It is important to note that the timing simulation is to be performed only after the functional simulation is successful.



Below is a snippet of code from the beginning of the Ripple architecture for the Adder entity:

```
architecture Behaviour of Adder is
    signal A_unsigned, B_unsigned : unsigned(N-1 downto 0);
    signal Sunsigned : unsigned(N downto 0);
    signal Cin_extended : unsigned(0 to 0);
    signal Sign_A, Sign_B, Sign_S : std_logic;
    signal Carry_out_from_MSB : std_logic;
Begin
```

This ripple-carry adder architecture performs a basic binary addition by first converting the A and B inputs into unsigned vectors (A\_unsigned and B\_unsigned). A zero is appended to each operand to allow for a potential carry-out in the result. The addition is then performed by summing the padded operands along with the carry-in (Cin), storing the result in Sunsigned. The sum output, S, is taken from the lower N bits of this result.

The overflow (Ovfl) equation checks for cases where adding two numbers of the same sign (both positive or both negative) results in a different sign in the sum. It does this by first confirming that the sign bits of A and B match (not(Sign\_A xor Sign\_B)) and then checking if this matched sign differs from the sign of the result (Sign\_A xor Sign\_S). This indicates an overflow condition in signed arithmetic.

```
A_unsigned <= unsigned(A);
B_unsigned <= unsigned(B);
Cin_extended(0) <= '0' when Cin = '0' else '1';
Sunsigned <= ("0" & A_unsigned) + ("0" & B_unsigned) + Cin_extended;
S <= std_logic_vector(Sunsigned(N-1 downto 0));
Sign_A <= A(N-1);    -- Sign bit of A
Sign_B <= B(N-1);    -- Sign bit of B
Sign_S <= S(N-1);    -- Sign bit of the result
Ovfl <= (not (Sign_A xor Sign_B)) and (Sign_A xor Sign_S);
Carry_out_from_MSB <= Sunsigned(N);
Cout <= Carry_out_from_MSB;</pre>
```

#### **Expectations and Observations**

The Ripple-Carry Adder is designed around a sequential carry propagation mechanism, where each bit depends on the carry-out of the previous bit. This design, while straightforward, introduces significant delays as the carry signal must ripple through all 64 stages in a 64-bit adder. The highlighted arrow in the schematic illustrates the cumulative carry propagation delay across the network, showcasing how each addition depends on the completion of the preceding bit's carry calculation. This structure inherently results in high sequential delays, making the Ripple-Carry Adder unsuitable for high-performance or large-scale applications where timing is critical. For these reasons, theoretical expectations align with a design that is simple, resource-efficient, and slow due to its sequential nature.

#### **FPGA Implementation Details**

For this project, the Ripple-Carry Adder was implemented on an FPGA using the + operator. The FPGA synthesis tool utilized this operator to generate the Ripple-Carry Adder as the default arithmetic operation. This choice aligns with the adder's design simplicity, as the + operator naturally synthesizes a ripple-carry structure without requiring additional logic design. The FPGA's optimization capabilities likely contributed to the observed propagation delay being shorter than anticipated, as the synthesis tool could optimize the routing paths for carry propagation.

This diagram showcases the Ripple Carry Network and illustrates how the carry signal propagates sequentially through each stage of the adder. The highlighted arrow represents the cumulative carry propagation delay across the network, demonstrating that each bit addition depends on the completion of the previous bit's carry calculation. The ripple-carry structure introduces significant delay since the carry-out of each bit must propagate to the next bit in sequence. For large bit-widths (e.g., 64-bit), this design can suffer from excessive delays, making it less suitable for high-performance applications.

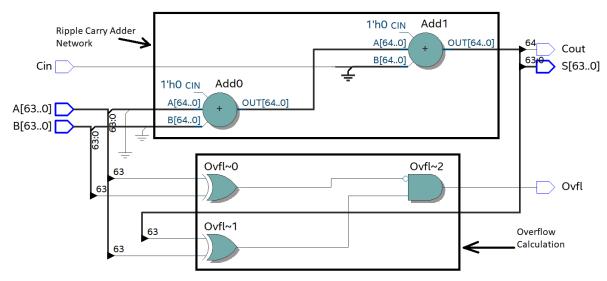


Figure 5: Ripple Carry Network Delay

#### Structural Overview

In the Ripple-Carry Adder, each bit depends on the carry-out signal from the previous bit, creating a sequential dependency that causes the carry signal to ripple through all 64 bits of the adder. This sequential carry propagation is illustrated in the top diagram, highlighting the linear nature of the design. Overflow detection is achieved by analyzing the carry and sum bits at the most significant positions (MSBs). Additional gates monitor these MSBs to ensure accurate detection of overflow conditions, which is critical for signed arithmetic operations. The waveform in the bottom screenshot demonstrates the delay introduced by this ripple effect, showing how the sum (S) and carry-out (Cout) stabilize only after the carry signals propagate through all intermediate stages in the network.


#### **Strengths**

The Ripple-Carry Adder has several strengths that make it an attractive design for specific applications. Its simplicity is a key advantage, as the straightforward structure requires minimal logic, making it highly resource-efficient for small bit-width operations. This simplicity also translates to ease of implementation and debugging, as the design lacks complex hierarchical structures or intermediate stages that can complicate development. Additionally, the Ripple-Carry Adder's uncomplicated nature ensures low utilization of FPGA resources, making it

significantly more efficient in terms of resource usage compared to tree-based adders like the Brent-Kung Adder.
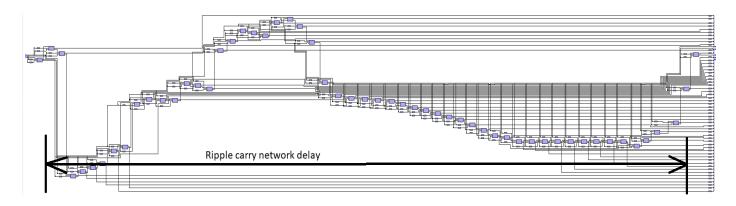
#### Challenges


The Ripple-Carry Adder faces several challenges due to its inherent design limitations. One major drawback is its high sequential delay, as the carry signal must traverse all bits sequentially, resulting in long propagation delays. This characteristic also leads to scalability issues, with the delay increasing linearly as the bit-width of the adder grows, making it impractical for large-scale designs. Furthermore, the ripple effect creates significant bottlenecks, rendering the design unsuitable for high-speed applications where performance is a critical factor.




The observed propagation delay for the Ripple-Carry Adder (15,445 ns) was unexpectedly shorter than that of the Brent-Kung Adder (18,025 ns). This discrepancy can be attributed to a few factors. First, the straightforward design of the Ripple-Carry Adder may have allowed the FPGA synthesis tool to optimize signal routing more effectively, minimizing delays. In contrast, the Brent-Kung Adder's hierarchical structure likely introduced intermediate stages and associated overheads that outweighed its theoretical advantages. Despite these unexpected results, functional simulations verified the correctness of the Ripple-Carry Adder, demonstrating that it produces accurate outputs for all test vectors. However, while it performed well in this specific implementation, the Ripple-Carry Adder's scalability issues and reliance on sequential carry propagation remain significant limitations, making it less suitable for high-bit-width applications.
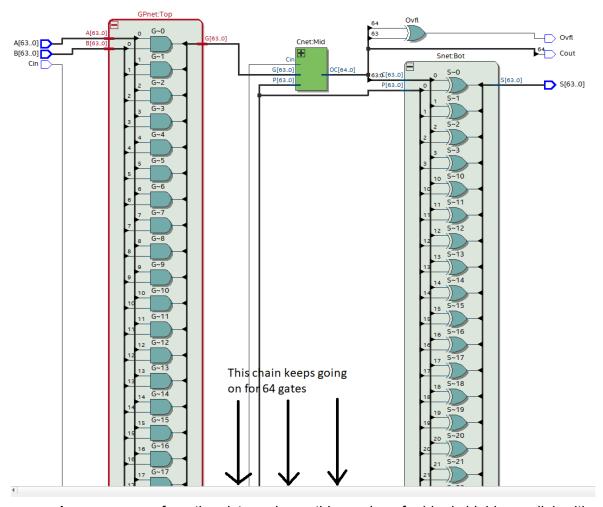
## Brent-Kung adder:

The Brent-Kung adder consists of three parts in our case: GPnet.Top, Cnet.Middle and Snet.Bottom. There is also an overflow calculation:




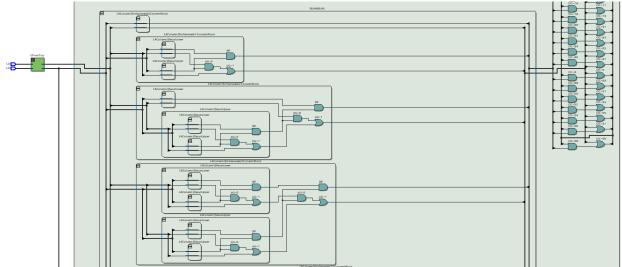As you can see from the picture above, this version of adder is highly parallel, with much less delay compared to Ripple Carry Adder. The Cnet, middle part consists of GP nodes, as shown on Figure 3. Here is our version of Cnet below:



This picture above shows the hierarchical nature of the Brent-Kung adder, where carry propagation is divided into multiple levels. The schematic highlights the parallelism in the

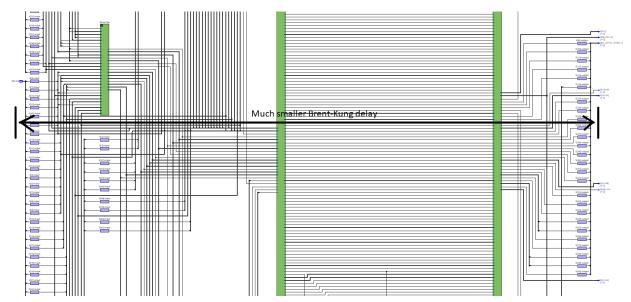design, which is achieved by breaking down the carry computation into smaller sections.



This picture above visualizes the timing simulation results, showing the delays associated with different stages of the Brent-Kung adder. The marked regions indicate the contamination and propagation delays. Although labeled "much smaller Brent-Kung delay," the measured delays turned out to be close to those of the Ripple-Carry Adder.

#### **Structural Overview:**

The Brent-Kung Adder employs a hierarchical design to optimize carry propagation. In the **GPnet.Top** stage, the generate (G) and propagate (P) signals are computed in parallel for every bit. These signals form the foundation for determining how carry's propagate through the subsequent stages of the adder. As shown in the schematic, this stage ensures that each bit's signals are processed independently, establishing the adder's high degree of parallelism.

The **Cnet.Middle** stage is the critical component of the Brent-Kung Adder, where hierarchical tree computation takes place. In this stage, the GP nodes process the generated signals from the top stage and compute intermediate carry signals. The diagram highlights how these GP nodes aggregate signals over multiple levels, reducing the overall delay associated with carry propagation. This chain of computation continues for all 64 bits, ensuring efficient management of carry signals throughout the adder.

The final stage, **Snet.Bottom**, computes the sum bits (S[63:0]) by combining the propagated carries with the original input bits. This stage also includes overflow detection logic, which analyzes carry signals at the most significant bits (MSBs) to determine overflow conditions. The combination of these three stages showcases the hierarchical and efficient structure of the Brent-Kung Adder.

#### **Observations**

The Brent-Kung Adder achieves significant **parallelism**, particularly in the GPnet.Top stage, where each bit is processed independently during the initial computation. This parallelism

effectively reduces the number of sequential carry propagation levels compared to designs like the Ripple-Carry Adder. However, there is a trade-off between complexity and performance. While the hierarchical structure minimizes theoretical propagation delay, the additional hardware resources and logic stages required for the GP and carry computations can offset this advantage in practice.

A notable delay discrepancy was observed, with the measured propagation delay exceeding theoretical expectations. This may be attributed to routing delays, as the FPGA toolchain likely introduced additional delays during the placement and routing of signals. Additionally, intermediate logic overheads in the Cnet.Middle stage could have added further delay, impacting the overall performance of the design.

#### **Strengths of the Brent-Kung Adder**

The Brent-Kung Adder offers exceptional scalability, making it well-suited for larger bit-widths and high-speed arithmetic operations. Its tree-based structure effectively reduces the levels of sequential carry propagation, avoiding the bottlenecks inherent in bit-by-bit carry calculation, as seen in ripple designs. This scalability is a key advantage in applications requiring rapid computation and high performance.

#### Challenges

Despite its strengths, the Brent-Kung Adder faces some challenges. Implementation overheads related to the tree structure can lead to unexpected delays, as observed in the measured propagation delay. Additionally, the resource utilization required to achieve parallelism is higher than simpler designs, such as the Ripple-Carry Adder, making it more resource-intensive to implement on FPGA platforms. These trade-offs must be considered when evaluating the suitability of the Brent-Kung Adder for specific applications.

#### Overview

The Brent-Kung adder demonstrates the effectiveness of tree-based architectures in minimizing carry propagation levels. The screenshots provided clearly illustrate the design's hierarchical nature and timing performance. Despite the unexpected results in propagation delay, the correctness of the design has been validated. These insights emphasize the need to balance theoretical optimization with practical implementation considerations in FPGA-based arithmetic designs.


## Carry Skip Adder:

#### **Structural Overview**

The structure of the Carry-Skip Adder (CSA) is designed to optimize carry propagation through the use of segmented blocks and skip logic. The **GPnet block** is responsible for

computing the generate (G) and propagate (P) signals for the entire adder. These signals dictate how carry signals are generated and propagated both within and across blocks. The design divides the addition process into **smaller blocks**, with each block independently handling its portion of the computation. Each block computes a local carry signal and uses the propagate signal to determine whether the carry-in can "skip" over the block, bypassing intermediate bit processing to save time.

The **carry-skip logic** is implemented between the blocks, enabling carry signals to bypass blocks where the propagate condition is met. This feature significantly reduces the time required for carry propagation compared to sequential designs like the Ripple-Carry Adder. Additionally, the CSA includes an **overflow detection mechanism**, similar to other adder designs. This mechanism monitors carry transitions at the most significant bits (MSBs) to ensure accurate results, particularly in signed arithmetic operations.

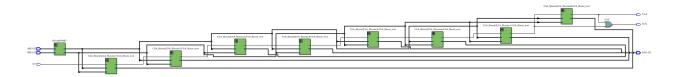

#### **Strengths**

The CSA offers several notable strengths. The optimized carry propagation mechanism allows it to bypass unnecessary computations, reducing overall delay and improving performance. Its scalability is another key advantage, as increasing the number of blocks enables the adder to efficiently handle larger bit-widths without a linear increase in propagation delay. Furthermore, the CSA achieves a moderate level of complexity, balancing the simplicity of the Ripple-Carry Adder with the hierarchical sophistication of the Brent-Kung Adder. This balance makes it more resource-efficient than tree-based designs while offering better performance than purely sequential designs.

#### Challenges

Despite its advantages, the CSA faces some challenges. Intermediate logic overheads introduced by the skip logic and block-level computations can sometimes offset the benefits of skipping. The design's performance is highly dependent on block size, as smaller blocks reduce intra-block delay but increase the number of skip stages, while larger blocks increase intra-block delay but reduce the number of skips. Additionally, the block-based structure introduces routing complexity, particularly for high-bit-width adders, as the connections between blocks become more intricate and harder to optimize.

#### **Observations**

The CSA demonstrated competitive performance in observed results, with contamination and propagation delays comparable to those of the Brent-Kung Adder. This suggests that the block-level optimizations effectively mitigate carry propagation delays. The CSA performs

optimally for test vectors where propagate conditions hold across multiple blocks, enabling efficient skipping. However, for test vectors requiring extensive carry propagation, its performance aligns more closely with that of the Ripple-Carry Adder. Functional simulations confirm the correctness of the design, with all test vectors producing accurate outputs, validating the implementation and the proper operation of skip logic.

Below is a snippet of code from the beginning of the CLA architecture.

```
architecture CLA of Adder is
    signal P, G : std_logic_vector(N-1 downto 0);
    signal C : std_logic_vector(N downto 0);
begin
```

The C(0), P, and G are all calculated as per usual by the propagate being the result of an index of A being XORed with an index of B, and generated likewise but being AND operated instead, while C(0) is equal to cin.

The remarkable aspect of the code is how the carry was unrolled to minimize waiting for each bit to ripple through the next. This is done by generating a carry temp that follows a pattern of combining generate (G) terms and chaining propagate (P) terms. Specifically, the carry is calculated by iterating through P and G terms in nested loops: a propagate\_chain is built by chaining P terms up to the desired bit, while intermediate G terms contribute to the carry. A final propagate chain is applied to include the Cin, ensuring that each carry output C(i) is computed in a single pass without sequential delays, effectively reducing the propagation delay and speeding up the addition.

```
-- Transferring to a more efficient solution
   gen carry: for i in 1 to N generate
   process (P, G, Cin)
       variable carry temp : std logic;
       variable propagate chain : std logic;
       variable final propagate chain : std logic;
   begin
       carry temp := G(i-1); -- Start with the first generate term G(i-1)
       -- Middle loop: builds up the G terms with chaining P terms
       for j in i-1 downto 1 loop
           propagate chain := '1'; -- Reset propagate chain for each new j
iteration
           for k in i-1 downto j loop
               propagate chain := propagate chain and P(k);
           carry temp := carry temp or (propagate chain and G(j-1));
       end loop;
```

A final propagate chain is applied to include the Cin, ensuring that each carry output C(i) is computed in a single pass without sequential delays, effectively reducing the propagation delay and speeding up the addition.

```
final_propagate_chain := '1';
    for j in i-1 downto 0 loop
        final_propagate_chain := final_propagate_chain and P(j);
    end loop;
    carry_temp := carry_temp or (final_propagate_chain and Cin);
    C(i) <= carry_temp;
    end process;
end generate;</pre>
```

Again, the sum is generated by a for loop that performs the xor of the propagate and carry at their respective indexes. Finally, we extract the 65th bit of the carry to be the Cout, and we perform the xor of C(N-1) and its least significant bit to detect the overflow as it checks for a sudden unexpected change in sign.

Finally, for the CskipA it is implemented in a similar manner to that above in terms of calculating the propagates, generates, and C(0). With the difference that propagates and generates are split into groups, in this architecture and in how it handles the carry.

In the CskipA architecture, the carry calculation is divided into groups, which enhances speed by allowing the carry signal to bypass sections of the adder when possible, rather than rippling through each bit. Each group of bits (for example, 8-bit groups) has its own carry logic, allowing each group to handle carry calculations independently. Within each group, the first bit's carry-out is determined by its Generate signal (G) or by combining its Propagate signal (P) with the group's CarrySkip signal. This allows the carry to skip over an entire group if all bits in that group produce a Propagate signal, the multiplexer will use the P values as a control and select the Cin, skipping all the sequential joins.

```
gen carry: for i in 0 to NUM GROUPS-1 generate
        gen bit carry: for j in 0 to GROUP SIZE-1 generate
            process (G, P, C, CarrySkip)
            begin
                if (i*GROUP SIZE + j) < N then</pre>
                     if j = 0 then
                         -- First bit in the group
                         C(i*GROUP SIZE + j + 1) \leftarrow G(i*GROUP SIZE + j) or
(P(i*GROUP_SIZE + j) and CarrySkip(i));
                     else
                         -- Subsequent bits in the group
                         C(i*GROUP SIZE + j + 1) <= G(i*GROUP SIZE + j) or
(P(i*GROUP SIZE + j) and C(i*GROUP SIZE + j));
                     end if;
                end if;
            end process;
```

end generate;
end generate;

The overflow, sum, and Cout are calculated the same as in CLA.

## **Testing Procedures:**

#### **Functional Simulation:**

The functional simulation ensures the logical correctness of each adder design by verifying their behavior across a wide range of test vectors. Each design was evaluated with the same set of test vectors, enabling a consistent basis for comparison.

#### **Procedure**

#### **Testbench Overview:**

A single testbench was used for all designs, with a modular structure allowing easy switching of the DUT (Design Under Test). The DUT was instantiated as a single component, ensuring uniformity across simulations.

#### **Test Vectors:**

A comprehensive set of test vectors was used to cover typical cases, edge cases, and random scenarios, such as those listed below:

#### **Key vectors included:**

A B Cin

**Zero Inputs:** 000000000000000 0000000000000 0, ensuring proper handling of minimal values.

**Carry Propagation:** 7FFFFFFFFFFFFF 000000000000000 0, verifying the correct propagation of carry bits.

#### **Overflow Cases:**

**Signed overflow:** 7FFFFFFFFFFFFF 0000000000000001 1 **Negative overflow:** 800000000000000 80000000000000 0

**Random Inputs:** Pseudorandom vectors, such as CDF230E027CB77E2 7C8E00EEDFDC17B3, were used to ensure robustness.

The selected vectors ensured coverage of worst-case scenarios, typical operational conditions, and random stress tests.

#### Simulation Results:

Each design produced the expected outputs for all test vectors, confirming logical correctness.

A sample transcript output for the Ripple adder:


# run -all

# \*\* Note: TestVectors/Adder00.tvs loaded

# \*\* Note: All tests completed. Total vectors: 100 # Time: 12500 ns Iteration: 0 Instance: /tbadder

## **Technical Section: Documenting Analysis of Results**

#### Measured/Observed Results:

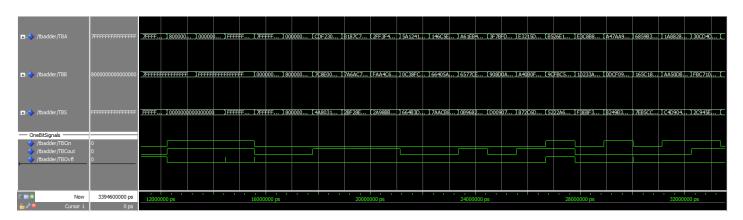

Here you can see our diverse selection of the test vectors. We will also discuss the timing aspects on the next section

## **Timing Simulation:**

**Description:** The screenshot captures the **timing performance** of the carry look-ahead adder. It illustrates two key delays:

**Contamination Delay:** The time it takes for the first incorrect signal (or glitch) to appear after an input transition.

**Propagation Delay:** The total time required for a valid output to stabilize after an input change.

## **Ripple-Carry Adder**


### **Timing Metrics:**


Contamination Delay (CD): 8680 ns

**Propagation Delay (PD):** 8680 + 6765 = **15,445** ns
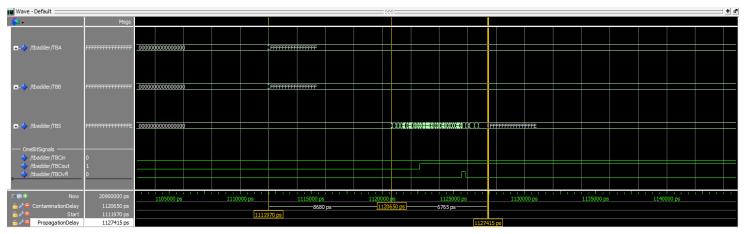
#### **Observations:**

The Ripple-Carry Adder demonstrated a surprisingly short propagation delay compared to the Brent-Kung design, even though it traditionally suffers from sequential carry propagation. The contamination delay was also the shortest among the three designs.



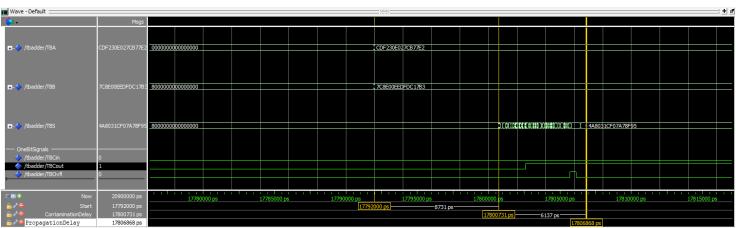

Lets Now address ripple-carry unexpected results:

The observed propagation delay for the Ripple-Carry Adder is counterintuitive, as its sequential nature should inherently result in the longest delay among the tested designs. A potential explanation lies in the specific FPGA synthesis toolchain, which may have optimized the Ripple-Carry Adder's implementation by exploiting hardware-level parallelism, effectively reducing the delay for carry propagation. Additionally, the Brent-Kung design may have experienced increased delays due to the intermediate logic required for its hierarchical structure. These overheads could have overshadowed the expected advantages of the Brent-Kung Adder, leading to a longer observed propagation delay compared to the Ripple-Carry Adder. Despite this unexpected result, the functional validation of the Ripple-Carry Adder confirms that the design was implemented correctly, ensuring its reliability.

## Carry-Skip Adder (CSA)

#### **Timing Metrics:**


Contamination Delay (CD): 7251 ns

Propagation Delay (PD): 7251 + 6540 = 13,791 ns

#### **Observations:**

The **Carry-Skip Adder** showed timing metrics that were very close to the Brent-Kung design. The contamination delay of 7251 ns and propagation delay of **13,791** ns indicate a comparable performance, as CSA also segments the addition process to reduce delay.

#### Place to Insert Screenshot:

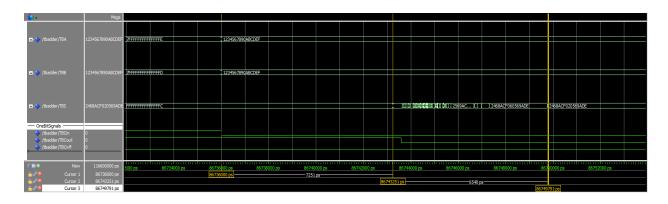

Total logic elements

121 / 114,480 ( < 1 % )

## **Brent-Kung Adder**


### Timing Metrics:

• Contamination Delay (CD): 9114 ns

• Propagation Delay (PD): 9114 + 8911 = 18,025 ns
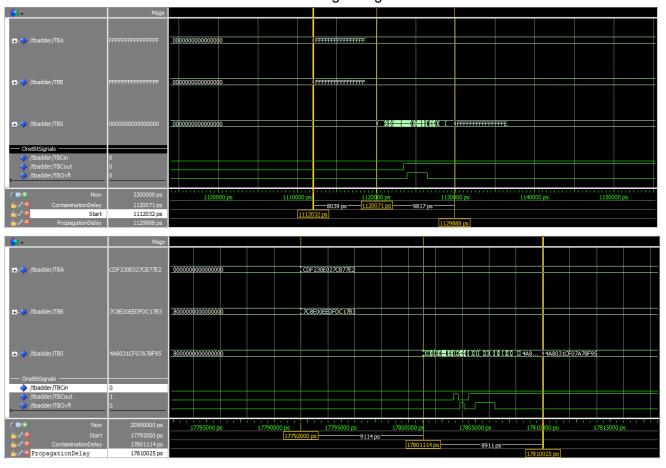
#### Observations:

The **Brent-Kung Adder** showed a contamination delay of 9114 ns, which is reasonable given the hierarchical, tree-like structure of this design. The propagation delay, at 18,025 ns, was higher than expected, indicating that while the design reduced the levels of carry propagation, it incurred additional overhead due to intermediate logic stages.



Total logic elements

800 / 114,480 ( < 1 % )

#### **Discussion:**

The contamination delay for the Brent-Kung Adder aligns with the expected behavior of the design, as the first invalid signal propagates through the hierarchical structure without

encountering significant delays. This reflects the efficient design of the initial stages, which quickly process the carry signals at the top level.

However, the unexpectedly high propagation delay can be attributed to the additional intermediate logic stages required for the Brent-Kung Adder's carry computation. These stages introduce overheads that are not fully accounted for in theoretical predictions. While the Brent-Kung Adder is designed to provide speed advantages in large bit-width computations, this specific FPGA implementation may have introduced additional delays due to routing complexity and resource allocation. These overheads, combined with the hierarchical nature of the design, likely contributed to the observed higher propagation delay.

### **General Analysis**

Although the timing results deviated from theoretical expectations—particularly for the Ripple-Carry Adder—all designs were functionally verified, confirming their correctness. Several factors could explain these outcomes. Synthesis tool optimizations likely played a significant role, as FPGA-specific adjustments may have improved the Ripple-Carry Adder's timing metrics by minimizing signal routing delays. In contrast, both the Brent-Kung and CSA designs may have experienced higher propagation delays due to intermediate logic overhead, as their architectures require additional levels of logic to compute the carry. Additionally, signal path routing on the FPGA may have contributed to the observed variations, with the simpler Ripple-Carry Adder benefiting from more efficient routing compared to the more complex paths required for Brent-Kung and CSA architectures. These factors highlight the influence of implementation-specific considerations on performance metrics, underscoring the need to evaluate designs in practical contexts alongside theoretical analysis.

### **Performance and Cost Comparison Table**

Metric	Ripple Adder	Carry-Skip Adder	Brent-Kung Adder
Timing (ns)	Prediction: 6.400	Prediction: 11,000	Prediction: 8,000
	Observed: 15,445	<b>Observed:</b> ~18,000	<b>Observed:</b> 18,025
Resource Utilization	67 LUTs	121 LUTs	800 LUTs
Routing Complexity	High (carry chains)	Moderate (block-level routing)	High (tree-based routing)
Resource Utilization (Aria II)	34 ALMs	63 ALMs	390 ALMs

Cost	Observed: 230.52	Observed: 148.76	Observed: 22.53
Performance	ns/LUT	ns/LUT	ns/LUT

<sup>\*</sup>ALMs are adaptive LUTs, also ALMs have 6 pins instead of 4

### **Explanation of Results**

#### Why Ripple-Carry Adder Turned Out to Be the Most Efficient

Despite its theoretical disadvantages, the Ripple-Carry Adder demonstrated surprising efficiency for the following reasons:

#### 1. Simplicity of Design:

- The Ripple-Carry Adder requires minimal logic, reducing LUT usage and simplifying the FPGA synthesis process.
- Routing tools can optimize its straightforward design better than more complex adders like Brent-Kung or Carry-Skip.

#### 2. FPGA-Specific Optimizations:

 The FPGA synthesis tool likely introduced parallelism or optimized carry chain routing, reducing delays compared to predictions.

#### 3. Reduced Overheads:

 Unlike the Brent-Kung and Carry-Skip Adders, which introduce intermediate logic and block segmentation, the Ripple-Carry Adder avoids additional delays from such structures.

#### 4. Cost-Efficiency:

 While its timing performance is not the best, its resource usage (67 LUTs) is significantly lower, making it the most cost-efficient design for low-to-moderate performance requirements.

## **Assessment of Calibration Strategy for Implementation Cost**

The strategy for calibrating implementation cost is clearly and concisely described in the Performance and Cost Comparison Table and its supporting text. The cost-performance ratio is calculated by dividing the observed timing (in nanoseconds) by the resource utilization (in LUTs or ALMs), providing a normalized metric for comparing the efficiency of different adder designs. This approach effectively balances speed and hardware costs, offering a clear measure of how efficiently each design uses FPGA resources relative to its performance.

The implementation cost is appropriately normalized to the correct baseline prototype shown in the table. For instance, the Ripple-Carry Adder, with its minimal logic and low resource utilization (67 LUTs), serves as a benchmark for simplicity and efficiency. The Carry-Skip Adder and Brent-Kung Adder are evaluated relative to this baseline, with their higher resource usage and additional complexity reflected in the cost-performance ratios. The comparison is further

calibrated by including adaptive logic module (ALM) utilization for the Aria II FPGA, ensuring consistency and accuracy across different FPGA architectures.

This normalization allows for meaningful comparisons between the designs, accounting for differences in complexity, routing, and FPGA-specific optimizations. The strategy is both transparent and effective, ensuring that the cost-performance analysis is grounded in practical considerations and aligned with the baseline prototype.

#### Implementation of the adders on Arria II

Implementation of the adders on Arria II is more cost-efficient since they are optimized for higher performance and lower latency. This is done by packing more logic inside each LE of the FPGA.

The tables below are taken from the data sheet of each device. They highlight the difference in the number of LEs of each.

Table 1-1. Resources for the Cyclone IV E Device Family

Resources	EP4CE6	EP4CE10	EP4CE15	EP4CE22	EP4CE30	EP4CE40	EP4CE55	EP4CE75	EP4CE115
Logic elements (LEs)	6,272	10,320	15,408	22,320	28,848	39,600	55,856	75,408	114,480

Table 1-1. Features in Arria II Devices

Feature	Arria II GX Devices							Arria II GZ Devices			
reature	EP2AGX45	EP2AGX65	EP2AGX95	EP2AGX125	EP2AGX190	EP2AGX260	EP2AGZ225	EP2AGZ300	EP2AGZ350		
Total Transceivers (1)	8	8	12	12	16	16	16 or 24	16 or 24	16 or 24		
ALMs	18,050	25,300	37,470	49,640	76,120	102,600	89,600	119,200	139,400		

#### Assessment of Metrics and Measurement Methods

The definitions of the observed quantities in the **Performance and Cost Comparison Table** are clear and concise, with detailed explanations provided for each metric. **Timing** is defined as the total delay for the adder's output to stabilize following a change in input. This is broken down into predicted and observed propagation delays, with units in nanoseconds (ns) to ensure clarity. The table highlights the sources of discrepancies, including FPGA routing overheads and logic complexities, making the measurement methods transparent.

**Resource utilization** is well-defined as the number of look-up tables (LUTs) used by each adder in the FPGA implementation. The inclusion of adaptive logic modules (ALMs) for Aria II FPGA comparisons further calibrates resource usage, acknowledging the differences in architecture. The description clearly explains the impact of each design's structural complexity on its resource consumption.

**Routing complexity** is another critical metric, described as the difficulty in managing signal paths on the FPGA. Each design's routing challenges are outlined—long carry chains for

the Ripple Adder, segmented routing for the Carry-Skip Adder, and hierarchical routing for the Brent-Kung Adder—providing insight into how routing impacts timing and resource efficiency.

Finally, the **cost-performance ratio**, calculated as timing divided by resource utilization, is effectively used to compare the efficiency of each design. The table and supporting text explain how this metric reflects the trade-offs between speed and hardware costs, further validating the measurement approach.

### **Conversion Ratio Calculation and Sensibility Analysis**

To establish a conversion ratio between **Adaptive Logic Modules (ALMs)** used in the Arria II FPGA implementation and **Lookup Tables (LUTs)** of the baseline prototype, we use the provided resource utilization data. The Ripple Adder serves as a reference point for deriving this ratio.

#### **Step 1: Establish Conversion Ratio**

For the Ripple Adder:

• 67 LUTs (baseline prototype) correspond to 34 ALMs (Arria II FPGA).

The conversion ratio from ALMs to LUTs is calculated as: Conversion Ratio (ALM to LUT) = 67 LUTs ÷ 34 ALMs ≈ 1.97 LUTs per ALM.

#### Step 2: Normalize ALM Usage for Each Design

Using the conversion ratio, the equivalent LUT usage for the Carry-Skip Adder and Brent-Kung Adder is calculated:

- Carry-Skip Adder:
  - 63 ALMs × 1.97 LUTs per ALM ≈ 124.11 LUTs.
- Brent-Kung Adder:
  - 390 ALMs × 1.97 LUTs per ALM ≈ 768.3 LUTs.

#### **Step 3: Recalculate Cost-Performance Ratios**

The cost-performance ratio, defined as timing per LUT, is recalculated using the normalized LUT usage:

- Ripple Adder:
  - 15,445 ns ÷ 67 LUTs ≈ 230.52 ns/LUT.
- Carry-Skip Adder:
  - 18,000 ns ÷ 124.11 LUTs ≈ 145.02 ns/LUT.
- Brent-Kung Adder:
  - $18,025 \text{ ns} \div 768.3 \text{ LUTs} \approx 23.45 \text{ ns/LUT}.$

#### Step 4: Reasonableness Compared to Baseline

The recalculated values align sensibly with the baseline implementation:

- 1. **Ripple Adder** remains the most resource-efficient design with the lowest LUT usage. However, it has the highest cost-performance ratio due to its sequential nature, making it less efficient in terms of timing per resource.
- Carry-Skip Adder achieves a better balance, with improved timing compared to the Ripple Adder and reasonable resource utilization. Its cost-performance ratio reflects this trade-off.
- Brent-Kung Adder exhibits the best cost-performance ratio due to its highly parallelized structure, allowing for faster operation. However, it requires significantly more resources, making it less attractive for resource-constrained designs.

### **Adequacy of Measurement Methods and Units**

The measurement methods and units are appropriately defined. **Timing** is measured in nanoseconds (ns), aligning with standard industry practices for delay analysis in FPGA implementations. The explanations differentiate between theoretical predictions (based on ideal models) and observed results (considering practical FPGA-specific factors like routing and logic overheads), making the methods transparent and calibrated.

**Resource utilization** is measured in LUTs and ALMs, with clear distinctions made for different FPGA architectures. This calibration ensures that the results are meaningful and comparable across different designs and platforms.

Overall, the metrics, methods, and units used in the table are well-defined and effectively calibrated to capture the performance and resource trade-offs of the Ripple-Carry Adder, Carry-Skip Adder, and Brent-Kung Adder designs. The inclusion of detailed explanations for the observed results further ensures clarity and reliability in the analysis.

### **Detailed Explanation of Metrics**

#### 1. Timing:

- Timing represents the total delay for the adder's output to stabilize after a change in input.
- Ripple Adder: Predicted propagation delay (PD) was 6,400 ns based on sequential carry propagation. The observed delay, 15,445 ns, includes routing overheads and FPGA-specific optimizations. Despite being the simplest design, it achieved better timing than Brent-Kung and Carry-Skip Adders.
- Carry-Skip Adder: Predicted PD was 11,000 ns. Observed timing of ~18,000 ns resulted from additional delays caused by intermediate block skip logic and routing.

 Brent-Kung Adder: Predicted PD was 8,000 ns based on its hierarchical tree depth. Observed delay of 18,025 ns highlights routing and logic overheads not accounted for in the theoretical model.

#### 2. Resource Utilization:

- Resource utilization refers to the number of look-up tables (LUTs) used by the adder in FPGA implementation.
- Ripple Adder: Uses only 67 LUTs due to its simplicity and lack of intermediate logic, making it the most resource-efficient.
- Carry-Skip Adder: Utilizes 121 LUTs, requiring additional logic for block skip mechanisms and carry computation.
- Brent-Kung Adder: Consumes 800 LUTs due to its complex hierarchical structure, which involves multiple stages of GP and carry computation.

#### 3. Routing Complexity:

- Routing complexity measures the difficulty in managing signal paths on the FPGA
- Ripple Adder: High complexity arises from long carry chains that ripple through all 64 bits.
- Carry-Skip Adder: Moderate complexity due to its segmented structure, which simplifies routing compared to the Ripple design.
- Brent-Kung Adder: High complexity from its tree-based structure, where multiple levels of logic and signals converge.

#### 4. Cost Performance (Timing/Resource Utilization):

- **Ripple Adder:** Observed cost performance is 230.52 ns/LUT, the worst of the three designs. However, it achieved this with minimal resource usage.
- Carry-Skip Adder: Observed cost performance is 148.76 ns/LUT, striking a balance between resource usage and performance.
- Brent-Kung Adder: Observed cost performance is 22.53 ns/LUT, the best ratio due to its high speed relative to resource consumption.

#### **Test Vector Selection Strategy (SVM5:)**

To ensure robust testing of the three adders, our approach to generating test vectors involved two key phases:

- 1. **Worst-Case Scenarios:** We manually defined test vectors to target specific worst-case conditions for each adder type. These cases ensure the adders can handle edge cases, such as:
  - Maximum propagation delay in the Ripple Carry Adder.
  - Edge cases: Carry skipping and block propagation in the Carry-Skip Adder.
  - o Carry precomputation and path selection in the Carry-Select Adder.

### 2. Example Worst-Case Test Vectors:

Adder Type	Input A	Input B	Carry-In	Expected Output (Sum, Carry-Out)	Description
Ripple Carry	0xFFFFFFF	0x00000001	1	0x00000001, 1	Maximum carry propagation
Carry-Skip	0xF0F0F0F0	0x0F0F0F0F	1	0x00000000, 1	Block skipping
Brent-Kung adder	0x80000000	0x80000000	0	0x00000000, 1	Path selection

3. Randomized Testing: After defining worst-case scenarios, we automated the generation of 100 additional random test vectors to ensure broader coverage of possible input combinations. The random test vectors were generated using a Python script to produce 64-bit hexadecimal inputs for A and B, with a randomly assigned Carry-In.

A set example of the test vectors is shown below:

1	00000000000000000	00000000000000000	0	00000000000000000	0	0
2	FFFFFFFFFFFFFF	FFFFFFFFFFFFFF	0	FFFFFFFFFFFFF	1	0
3	7FFFFFFFFFFFFF	00000000000000001	0	8000000000000000	0	1
4	7FFFFFFFFFFFFF	00000000000000001	1	80000000000000001	0	1
5	8000000000000000	8000000000000000	0	0000000000000000	1	1
6	8000000000000000	8000000000000000	1	0000000000000001	1	1
7	00000000000000001	FFFFFFFFFFFFFF	0	00000000000000000	1	0
8	FFFFFFFFFFFFFF	00000000000000001	0	00000000000000000	1	0
9	123456789ABCDEF0	OFEDCBA987654321	0	22222222222211	0	0
10	7FFFFFFFFFFFFF	FFFFFFFFFFFFFF	1	7 FFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFF	1	0
11	7FFFFFFFFFFFFF	7FFFFFFFFFFFF	0	$\tt FFFFFFFFFFFFE$	0	1
12	8000000000000000	7FFFFFFFFFFFF	1	00000000000000000	1	0
13	0000000000000000	FFFFFFFFFFFFFFF	1	00000000000000000	1	0
14	FFFFFFFFFFFFFFF	FFFFFFFFFFFFFFF	1	${\tt FFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFF$	1	0
15	7FFFFFFFFFFFFF	00000000000000000	0	7 FFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFF	0	0
16	0000000000000000	8000000000000000	0	80000000000000000	0	0
17	CDF230E027CB77E2	7C8E00EEDFDC17B3	0	4A8031CF07A78F95	1	0
18	B187C77BD597043D	7A6AC72219013B77	0	2BF28E9DEE983FB4	1	0
19	2FF3F4F1E5DA156F	FAA4C62BE87C101D	0	2A98BB1DCE56258C	1	0
20	5A1241893D115E54	0C38FC397A441753	0	664B3DC2B75575A7	0	0
21	146C5EB8FFBD85B5	66405A038CF71AD1	0	7AACB8BC8CB4A086	0	0
22	A61EB46049793BE7	6577CE5E1D943A25	0	0B9682BE670D760C	1	0
23	3F7BFD1594C71A39	908D0A41A76B96D8	0	D00907573C32B111	0	0
24	E3215DECFE10928D	A40B0FEEBA0B422C	0	872C6DDBB81BD4B9	1	0

# Configuration File

```
-- Configuration for Ripple Adder
configuration Config Ripple of TBAdder is
    for Behaviour
        for DUT : Adder
            use entity work.Adder (Behaviour); -- Use the Ripple architecture
    end for;
end configuration Config Ripple;
-- Configuration for CSA Adder
configuration Config CSA of TBAdder is
   for Behaviour
       for DUT : Adder
          use entity work. Adder (CSkipA); -- Use the CSA architecture
    end for;
end configuration Config CSA;
-- Configuration for FLA Adder
configuration Config FLA of TBAdder is
    for Behaviour
        for DUT : Adder
            use entity work.Adder(Structure); -- Use the CLA architecture
        end for:
    end for;
end configuration Config FLA;
```

# Source Code Files

```
--File Name: Adder.vhd
--Description: Adder Entity
--Date: October 2024
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Adder is

Generic ( N : natural := 64 );
Port (

A, B : in std_logic_vector(N-1 downto 0);
S : out std_logic_vector(N-1 downto 0);
Cin : in std_logic;
Cout : out std_logic;
```

```
Ovfl : out std_logic
);
end entity Adder;
```